

# g55\_7\_segment\_decoder - Display Input as Hexadecimal or Card Value

Group 55

Juliette Regimbal (260657238)

Qingzhou Yang (260687570)

February 20, 2017

## 1 Circuit Description

The *g55\_7\_segment\_decoder* circuit takes a 4-bit input called `code` that stores an unsigned integer, and a 1-bit input called `mode` that sets if the output should be in hexadecimal (low) or if the number should be displayed as the equivalent card value in a standard deck (high). The output is a 7-bit active-low bus meant to be connected to a 7 segment display. Bit 0 goes to segment 0, bit 1 goes to segment 1, and so forth. Since the values in a deck of cards only goes up to 12 (a king), numbers greater in this will be displayed as a '-' in card mode. Since the number 10 exists in the card display, only the 0 is displayed.

The pinout for the circuit is as follows:

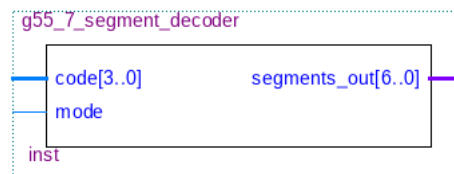


Figure 1: *g55\_7\_segment\_decoder* Pinout

## 2 Circuit Testing

The *g55\_7\_segment\_decoder* was tested for all possible inputs by combining the code and mode inputs into a single 5-bit word that was set from  $00000_2$  to  $11111_2$ . The output was recorded and verified by plotting it in ModelSim. The waveform out is as follows:

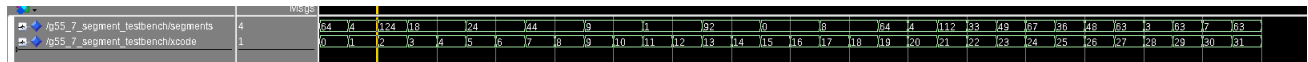


Figure 2: *g55\_7\_segment\_decoder* Test Wave