

g55_rules - Crazy Eights Legal Move Checker

Group 55

Juliette Regimbal (260657238)

Qingzhou Yang (260687570)

March 27, 2017

1 Circuit Description

The *g55_rules* circuit has two 6-bit inputs (`play_pile_top_card` and `card_to_play`) and one 1-bit output (`legal_play`). Based on the inputs, the circuit determines if the attempted move is legal in the game of Crazy Eights. Specifically it checks that `card_to_play` is a card of a value of 8, or a card of the same value as `play_pile_top_card`, or a card of the same suit as `play_pile_top_card`, or any suit and value if `play_pile_top_card` has a value of 8. The value and suit are encoded in 6-bit unsigned integer V where $V = (value - 1) + (suit * 13)$.

A pinout of the circuit is as follows:

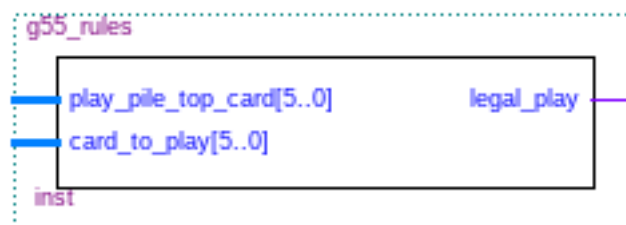


Figure 1: *g55_rules* Pinout

2 Testing

The circuit was tested using a timing simulation. Due to the high number of possible input patterns, inputs were chosen that both matched and failed each rule resulting in a true and false output respectively. The worst-case maximum propagation delay is 19.910 ns.

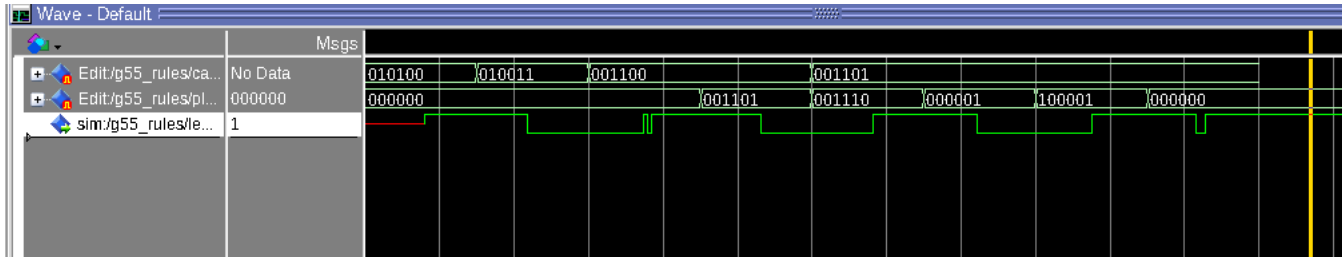


Figure 2: *g55_rules* Timing Simulation Results

3 FPGA

The *g55_rules* circuit uses a total of 40 logic elements representing less than 1% of the total available elements on the FPGA.